

```

clc;
close all;
clear all;
%-----For High pass constant-k Filter-----%

% shows error in publishing when we have to take inputs.
% Uncomment the below C ,L and f lines for Input from user.
C = input('Enter the Value of Capacitance in micro Farad:- ');
L = input('Enter the Value of Inductance in milli Henry:- ');
%f = input('Enter the value of Frequency in Giga Hertz: -');
% Here is f is not needed , we need the frequency for when we want to find
% Image Impedance

%C = 20; L = 5;
C = C * (10^(-6));
L = L * (10^(-3));
%f = f * (10)^9;
%omega = 2*pi*f;
%-----Cutoff Frequency-----%
omega_c = 1/(4*L*C)^(1/2);
%disp('Value of omega_c');
%disp(omega_c);
%disp('range of w');
w = linspace(0,3*omega_c,1000);

%-----Propogation Factor-----%

```

% $e_{\gamma} = 1 + \frac{z_1}{2z_2} + \left(\frac{z_1}{z_2} + \frac{z_1^2}{(2z_2)^2}\right)^{1/2}$ on solving in
% terms of ω and ω_c we get:-

```
e_gamma = zeros(1,length(w));
```

```
for k = 1 : length(w)
```

```
    e_gamma(k) = 1 - 2*((omega_c^2)/w(k)^2)  
    +((2*omega_c/w(k))*(((omega_c^2/w(k)^2) - 1)^(1/2)));
```

```
end
```

```
propogation_constant = log(e_gamma);
```

```
alpha = real(propogation_constant);
```

```
beta = imag(propogation_constant);
```

```
%-----Plot-----%
```

```
figure(1);
```

```
p = plot(w,alpha,w,beta,'r');
```

```
p(1).LineWidth = 2;
```

```
p(2).LineWidth = 2;
```

```
disp(p);
```


```
xline(omega_c,'-','\omega_c');
```

```
legend('\alpha','\beta','\omega_c');
```

```
title('\alpha and \beta VS \omega of a constant-k High pass filter');
```

```
xlabel('\omega');
```

```
ylabel('\alpha,\beta');
```

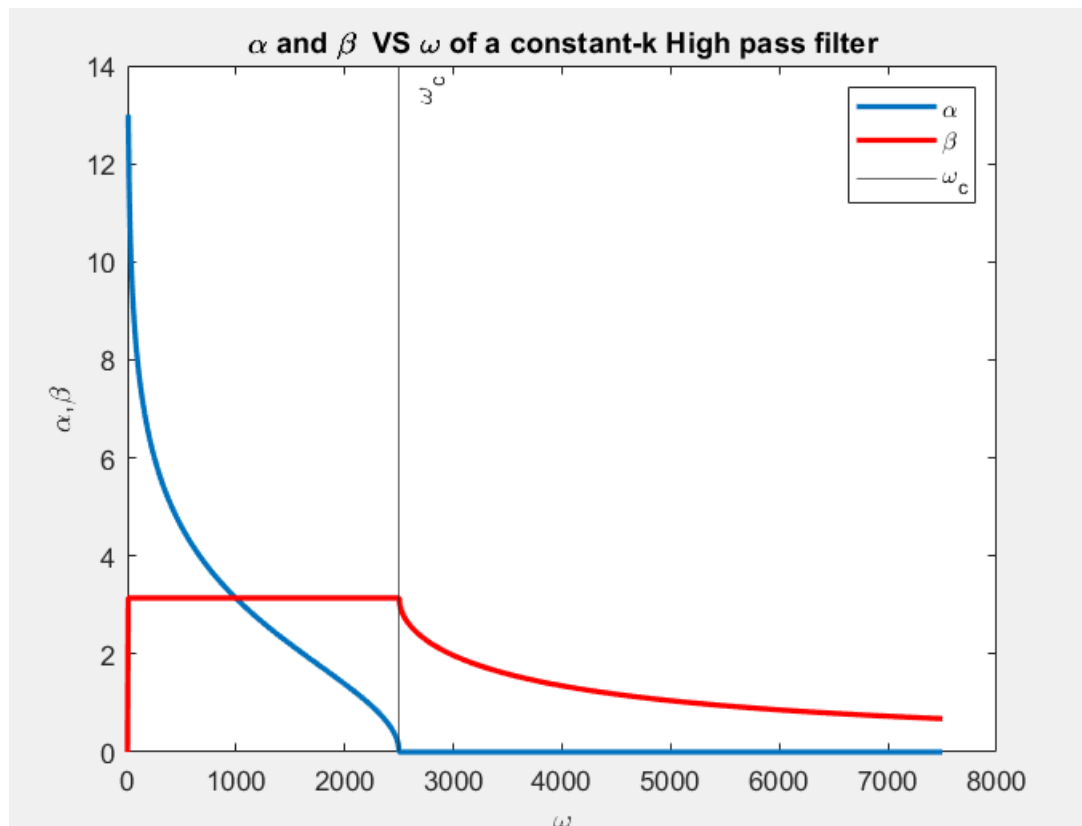

The above plot corresponds to the values $L = 20\text{mH}$ and $C = 2\mu\text{F}$